

F.Y.B.Sc. (Comp. Science) Semester - I
Regular Semester-End Examination
Session : Nov. 2022

Subject : Principles of Digital Electronics

Subject Code : USCSEL-112

Time : 2 Hrs.

Total Marks 35

- Instructions :**
- (1) All questions are compulsory.
 - (2) Figures to the right indicate full marks.
 - (3) Draw neat labelled diagram wherever necessary.
 - (4) Use of non programmable calculators are allowed.

Q.1 Attempt any Five of the following.

(5*1=5)

- (a) Write truth table of XOR gate.
- (b) Compute $(110101)_2 = (?)_{10}$.
- (c) Negate the number : 0111.
- (d) Write full form of ASCII.
- (e) Calculate $(1AC)_{16} = (?)_2$.
- (f) Name the universal logic gates.
- (g) Find the number of select inputs required for 16:1 multiplexer.

Q.2 Attempt any Five of the following.

(5*3=15)

- (a) Give the characteristic of a gray code and convert the following binary number to gray code
(i) 1110 (ii) 0110
- (b) Draw logic diagram of 1:2 demultiplexer. Also write its truth table.
- (c) Convert the following Boolean expression to standard SOP form.
 $y = AB + AC + \bar{C}$
- (d) Explain the parameter voltage level of a TTL logic family.
- (e) What do you mean by weighted and non-weighted code? Give one example of each.
- (f) Draw diagram of Half adder and also write its truth table.
- (g) Define the term :- (i) Encoder (ii) Parity bit

Q.3 Attempt any three of the following.

(5*3=15)

- (a) Draw diagram of parity generator circuit and explain its working.
- (b) Design the binary to gray converter circuit using K map.
- (c) State, draw symbol and prove any one DeMorgan's Theorem.
- (d) Draw diagram of OR gate constructed using NAND gates only.
- (e) Simplify the following expression using boolean laws and also draw the simplified diagram.
 $y = A(AB + AC) + \bar{A}(AB + \bar{A}B)$