

DEPARTMENT OF COMPUTER SCIENCE

B.Sc. (Comp. Sc.) Electronics (First Year)

Semester II EXAMINATION

Subject code: USCSEL 121

Paper Title: INSTRUMENTATION SYATEMS

Time: 2 Hours

Maximum marks: 35

Instructions to candidates:

1. All question are compulsory
2. Draw neat labelled diagram wherever necessary
3. Figure to the right indicate full marks
4. Use of non-programmable calculator is allowed

Q.1) Answer any five of the following:

[1x5=5]

- a. What is active sensor?
- b. Define actuator.
- c. State any two applications of Instrumentation system.
- d. State different types of motors.
- e. Which type of signal conditioning is required for thermistors?
- f. Write name of the temperature sensor IC.
- g. Draw symbol of operational amplifier.

Q.2) Answer any five of the following:

[3x5=15]


- a. Define the following with respect to OpAmp:
 - I. CMRR
 - II. input impedance
- b. Draw diagram of OpAmp as non-inverting amplifier and derive an expression for the output of this circuit.
- c. Draw neat block diagram of control system and explain.
- d. Define any three characteristics of a sensor. → sensitivity, linearity, accuracy
- e. Explain working principal of LDR with neat structure diagram. State material used and one application of LDR.

- f. What is motor? Draw diagram of construction of D.C. motor.
- g. If Op amp has common mode gain as 10 and differential mode gain 1000, find CMRR in dB.


Q.3) Answer any three of the following:

[5x3=15]

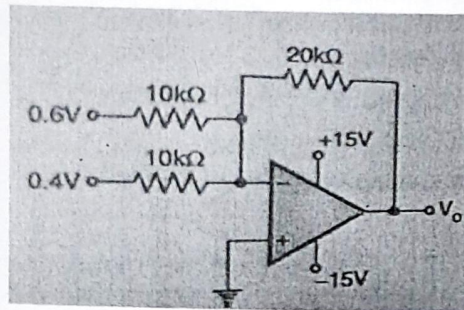- a. With the help of circuit diagram explain voltage to current converter.
- b. Explain working of stepper motor using neat, labeled diagram.
- c. Identify the following circuit and find output voltage of this circuit.



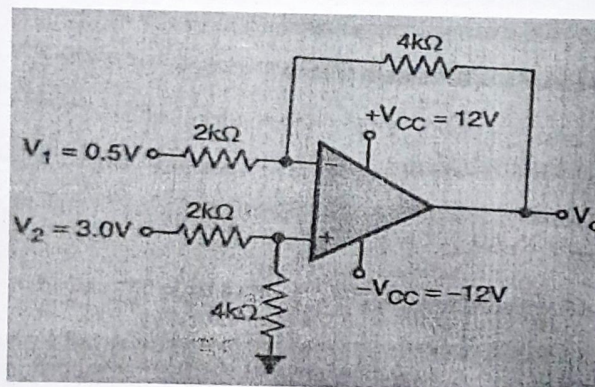- d. i) Identify the following circuit and find output voltage for the given input values in the circuit diagram.
- ii) If input values are changed to $V_1 = 1.0\text{ V}$ and $V_2 = 4.0\text{ V}$ what will be the output?



- e. With neat diagram explain principle of operation of ultrasonic sensor.